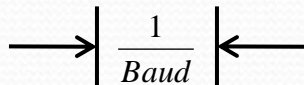


Exercise 12 (UART Transmitter)

- RS-232 signal phases
 - Idle
 - Start bit
 - Data (8-data for our project)
 - Parity (no parity for our project)
 - Stop bit – channel returns to idle condition
 - Idle or Start next frame




Baud rate will be 19200baud with 50MHz clock → 2604 divider → 12-bit




- Transmitter sits idle till told to transmit. Then will shift out a 9-bit (start bit appended) register at the baud rate interval.

Exercise 12 (UART Transmitter)

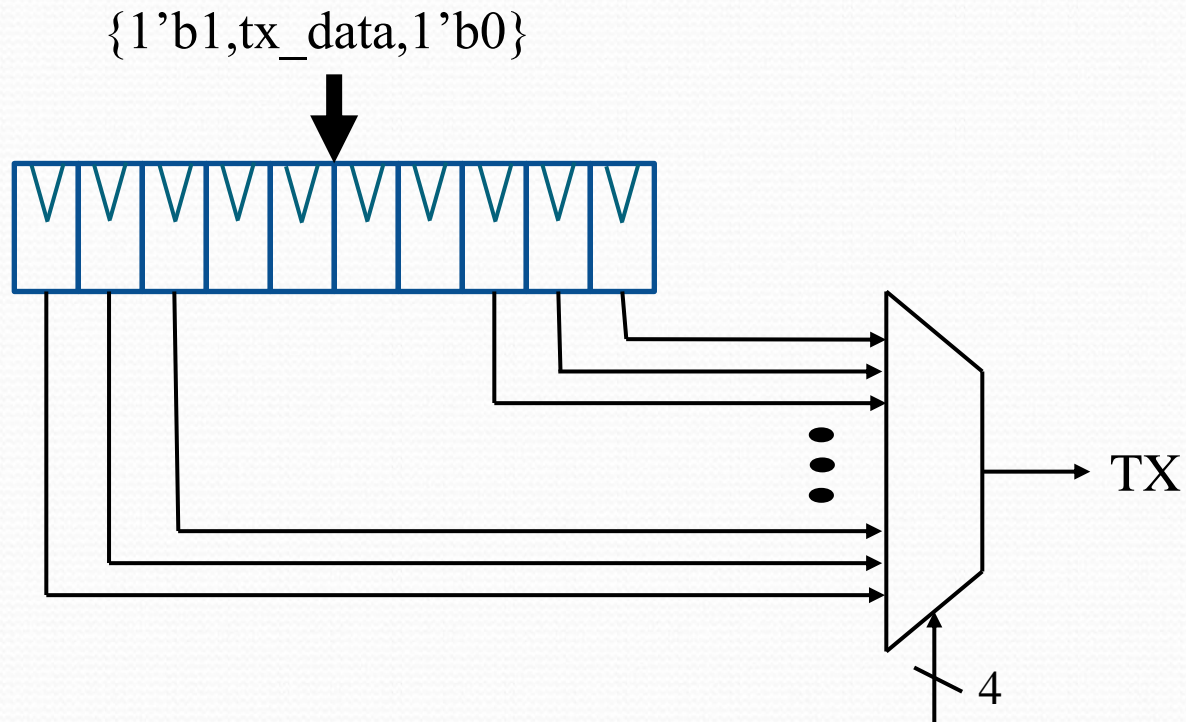


Exercise 12 (UART Transmitter)

$\{1'b1, tx_data, 1'b0\}$

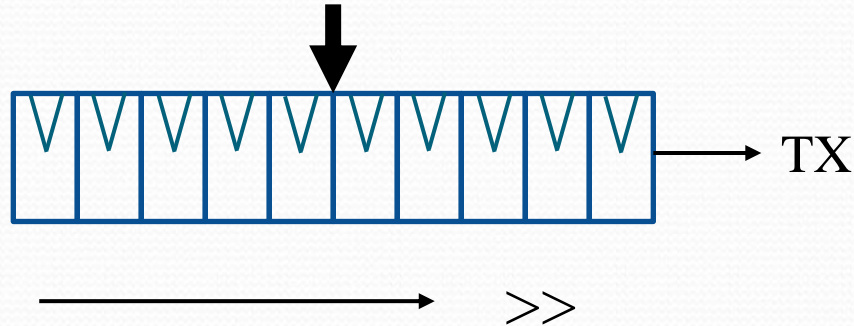


A simple shift reg is heart of the machine

$\{tx_data, 1'b0\}$

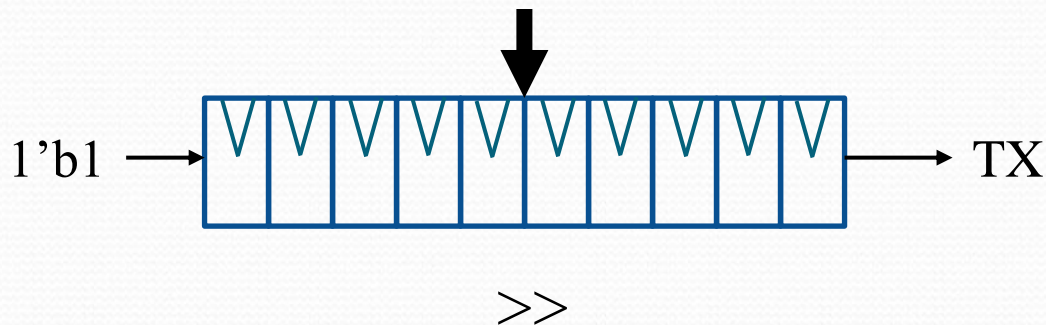


Does not even have to be 10-bits, can get away with 9.

Possible Topology of UART_tx

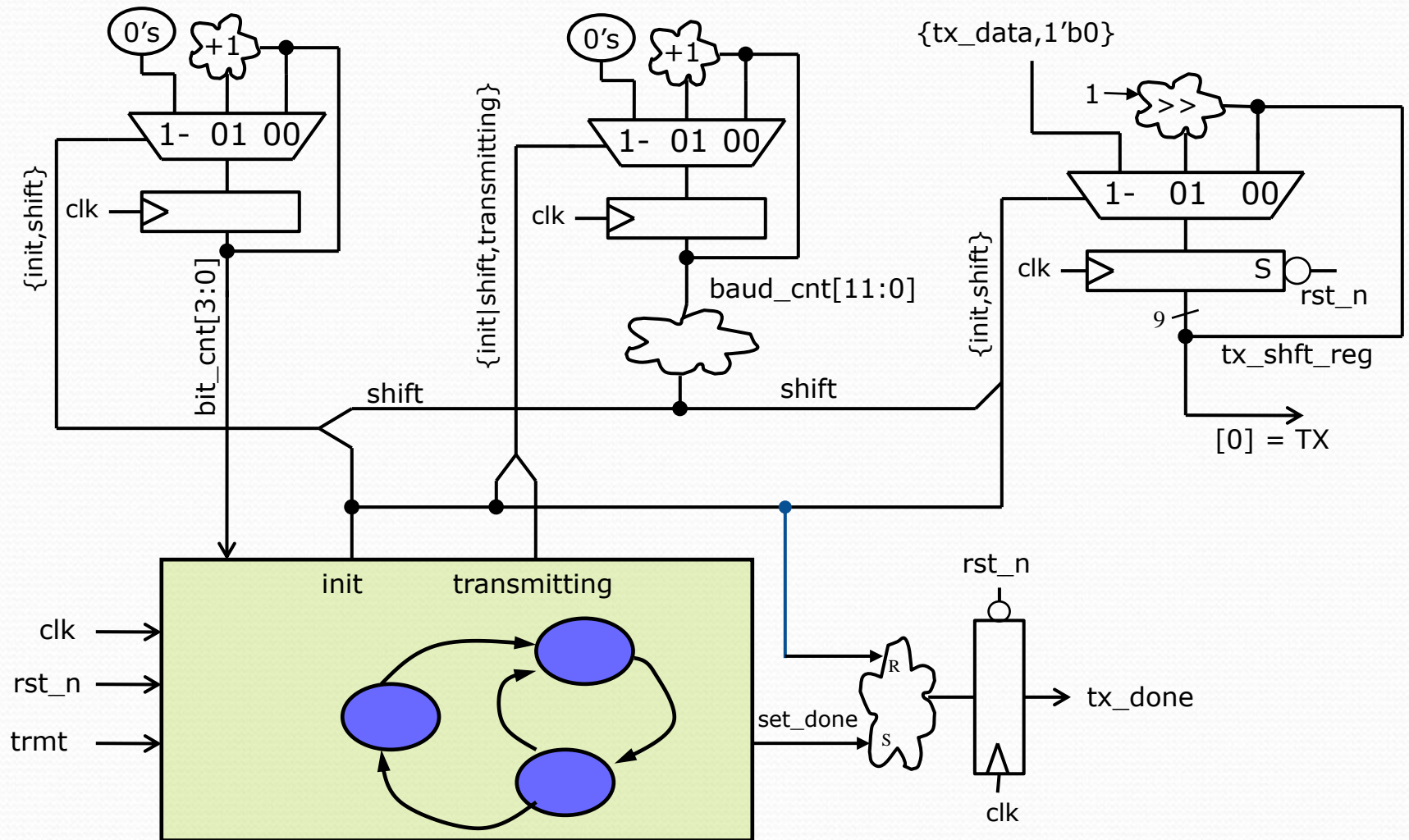

Exercise 12 (UART Transmitter):

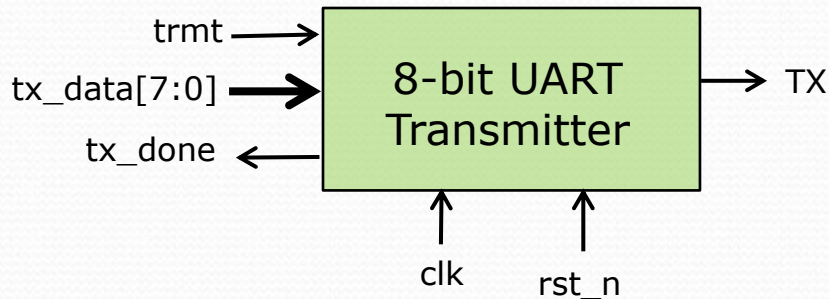

Signal:	Dir:	Description
clk,rst_n	in	50MHz system clock & active low reset
TX	out	Serial data output
trmt	in	Asserted for 1 clock to initiate transmission
tx_data[7:0]	in	Byte to transmit
tx_done	out	Asserted when byte is done transmitting. Stays high till next byte transmitted.

- HW3 Problem 3 involves making a UART transmitter (*UART_tx.sv*). You are to start that design during this exercise.
- Make a simple test bench for it. Just instantiate your transmitter and send a few bytes. Verify correct functionality (including baud rate) by looking at the waveforms.
- In Ex13 we will make *UART_rx*. Once we have both a transmitter and a receiver making a self checking testbench becomes trivial.
- Submit as much as you have done to the dropbox for Ex12. Wednesday we will look at UART receiver, and we have through Friday to finish transmitter/receiver.