


ECE 551

Digital Design And Synthesis

Fall '21

Synthesis Flow
Synthesis Optimizations

1

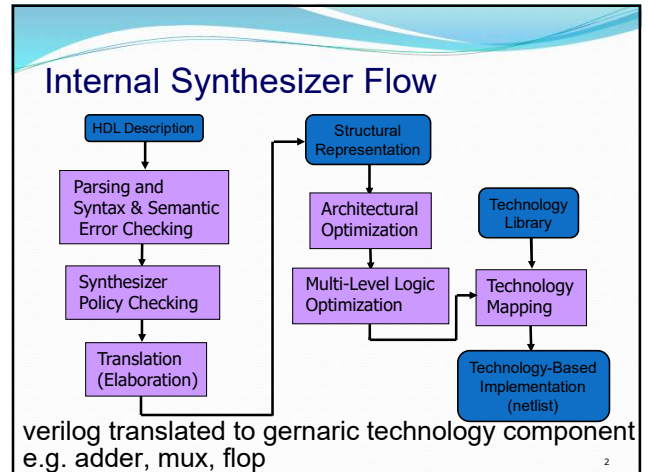

2

Initial Steps *(Analyze Verilog File)*

- Parsing for Syntax and Semantics Checking
 - Gives error messages and warnings to user
 - User may modify the HDL description in response
- Synthesizer Policy Checking
 - Check for adherence to allowable language constructs
 - This is where you find out you can't use certain Verilog constructs
- Allowed constructs can be synthesizer-dependent
 - Example: Design Vision allows indexed part-select (`guess[i+2 : 2]`), but the Xilinx tool does not
 - Certain things common to MOST synthesizers

3

Translation (Elaboration)

- Unrolls loops, substitutes macros & parameters, computes constant functions, evaluates generate conditionals
- Initial transformation to hardware.
 - Like a netlist, but includes larger components
 - Not just gate-level, may include adders, etc.
 - What you code is what you get.
 - Structural representation depends on HDL quality
 - Poor HDL can prevent optimization

4

Importance of Translation

- It is important for the tool to recognize the sort of logic structures you are trying to describe.
- If it sees a 32-bit full adder, the tool has built-in solutions for optimizing adders
 - Ripple-carry, carry-save, carry look-ahead, etc.
- If it just sees a Boolean function with 65 inputs, it has to work a lot harder to achieve the same results
 - Do you think it can invent a CLA on the fly?

5

5

Optimization in Synthesis

- Architecture choices made first (CLA,RCA,...)
- Try to detect unused states (logic states you can't get to)
- Boolean logic level optimization next
 - Detect and eliminate redundant logic
 - Exploit don't-care conditions
- Maps to cells from the technology library
- Attempts to meet all specified constraints
- Detect combinational feedback loops

6

6

Architectural Optimization

- Examples:
 - Replace an adder used as a counter with incrementor
 - Replace adder and separate subtractor with adder/subtractor if not used simultaneously
 - `if (~sub) z = a + b; else z = a - b;`
 - Performs selection of pre-designed components (Synopsys DesignWare)
 - adders, multipliers, shifters, comparators, muxes, etc.
- Need good code for synthesizer to do this
- Designer still knows more about the project

7

7


Logic/Gate-Level Optimization

- Mapping
 - Generates a gate level implementation
 - Tries to meet timing and area goals
- Delay optimization
 - Tries to fix delay violations from mapping phase.
 - Does not fix design rule violations or meet area constraints.
- Design rule fixing
 - Tries to correct design rule violations
 - Inserting buffers or resizing existing cells
 - If necessary, violates optimization constraints
- Area optimization
 - Tries to meet area constraints, which have lowest priority

8

8

Gate-Level Optimization

 

9

Logic Optimizations

- Area
 - Number of gates fewer == smaller
 - Fan in of gates (# inputs) fewer == smaller
 - Drive Strength (transistor width) narrower == smaller
- Delay
 - Number of logic levels fewer == faster (usually)
 - Fan in of gates (# inputs) fewer == faster
- Gate Effort → Summation of Fan in of gates needed to implement function

$$GateEffort = \sum fanin(gates)$$
- Note that examples that follow ignore NOT gates for gate count / levels of circuits

10

10

Logic Optimizations

- Decomposition
- Extraction
- Factoring
- Substitution
- Elimination
- You don't have to remember the names of these
- But understand the concept and the motivation

11

11

Decomposition

- Find common expressions
- Reduce redundancy
 - Reduce area (number/size of gates)
- May increase delay
 - More levels of logic

12

12

Decomposition Example

- $F = abc + abd + a'c'd' + b'c'd'$
~7 gates, ~3 levels
- $F = ab(c + d) + c'd'(a' + b')$
- $F = ab(c + d) + (c + d)'(ab)'$
- $X = ab$ 1 gate, 1 level
- $Y = c + d$ 1 gate, 1 level
- $F = XY + X'Y'$ 3 gates, 3 levels (or what?)
- Gate Effort = $4 \times (3\text{-input AND}) + 4\text{-input OR} = 16$ effort
- Gate Effort = $2\text{-input AND} + 2\text{-input OR} + 2 \times (2\text{-input AND}) + 2\text{-input OR} = 10$ effort

13

13

Extraction

- Find common sub-expressions in functions
- Like decomposition, but across more than one function
- Reduce redundancy
 - Reduce area (number/size of gates)
- May increase delay if more logic levels introduced

14

14

Extraction Example

- $F = (a + b)cd + e$ 3 gates, 3 levels
- $G = (a + b)e'$ 2 gates, 2 levels
- $H = cde$ 1 gate, 1 level
- Define common terms: $X = a + b$, $Y = cd$ 1 gate, 1 level (each)
- $F = XY + e$ 3 gates, 3 levels
- $G = Xe'$ 2 gate, 2 levels
- $H = Ye$ 2 gate, 2 levels
- Before:
 - (3) 2-input ORs, (2) 3-input ANDs, (1) 2-input AND
 - Gate Effort = $6 + 6 + 2 = 14$
- After
 - (2) 2-input ORs, (4) 2-input ANDs
 - Gate Effort = $4 + 8 = 12$

15

15

Factoring

- Traditional two-level logic is sum-of-products
- Sometimes better expressed by product-of-sums
 - Fewer literals => less area
- May increase delay if logic equation not completely factored (becomes multi-level)

16

16

Factoring Example

- Definitely good:
 - $F = ac + ad + bc + bd$ Gate Effort = $8 + 4$
 - $F = (a + b)(c + d)$ Gate Effort = $4 + 2$
- Maybe good:
 - $F = ac + ad + e$ Gate Effort = 7
 - $F = a(c + d) + e$ Gate Effort = 6
- Factoring may improve area...
- But will likely increase delay (tradeoff)

17

17

Substitution

- Similar to Extraction (in fact a sub-case of extraction)
- When one function is subfunction of another
- Reduce area
 - Fewer gates
- Can increase delay if more logic levels

18

18

Substitution Example

- $G = a + b$ 1 gate, 1 level
- $F = a + b + c$ 1 gate, 1 level
- $F = G + c$ 2 gate, 2 levels
- **Before:**
 - (1) 2-input OR, (1) 3-input OR \Rightarrow Gate Effort = 5
- **After**
 - (2) 2-input ORs (but increased levels) \Rightarrow Gate Effort = 4

19

19

Elimination (Flattening)

- Opposite of previous optimizations
- Goal is to reduce delay
 - Make signals travel through as few logic levels as possible
- But will likely increase area
 - Gate replication / redundant logic

20

20


Elimination Example

- $G = c + d$ 1 gate, 1 level
- $F = Ga + G'b$ 3 gates, 3 levels
- $G = c + d$ 1 gate, 1 level
- $F = ac + ad + bc'd'$ 4 gates, 2 levels
- **Before:**
 - (2) 2-input ORs, (2) 2-input ANDs
- **After:**
 - (1) 2-input OR, (1) 3-input OR, (2) 2-input ANDs, (1) 3-input AND (but fewer levels)

21

Sharing and Unsharing

 
- Expression sharing may be overridden later due to timing
 - $Z_1 \leq A + B + C$
 - $Z_2 \leq A + B + D$
 - Arrival time of A and B is less than D and C



22

Sharing and Unsharing

 - Mutually exclusive operations can share resources
 - if(SEL) $Z = A + B$
 - else $Z = C + D$



23