

Exercise 2: Structural Verilog *(Implement a ring osc)*

- You should have some familiarity with structural verilog. You used it to perform the AHW's in ECE 352.
- Structural Verilog is simply instantiation and wiring of cells/blocks whose functionality is known.
- The cells/blocks might be built in primitives (AND, OR, NOT, ...) or might be more complex cells that you defined using dataflow or behavioral verilog.

Exercise 2: Structural Verilog (*built in primitives*)


- Built in primitives: **AND, OR, NOT, NAND, NOR, XOR, XNR, BUFIF1, NOTIF1, BUFIF0, NOTIF0**
- Output port appears before input ports
- Optionally specify: instance name and/or delay

and N25 (Z, A, B, C); // name specified

and #10 (Z, A, B, X),
 (X, C, D, E); // delay specified, 2 gates

and #10 N30 (Z, A, B); // name and delay specified

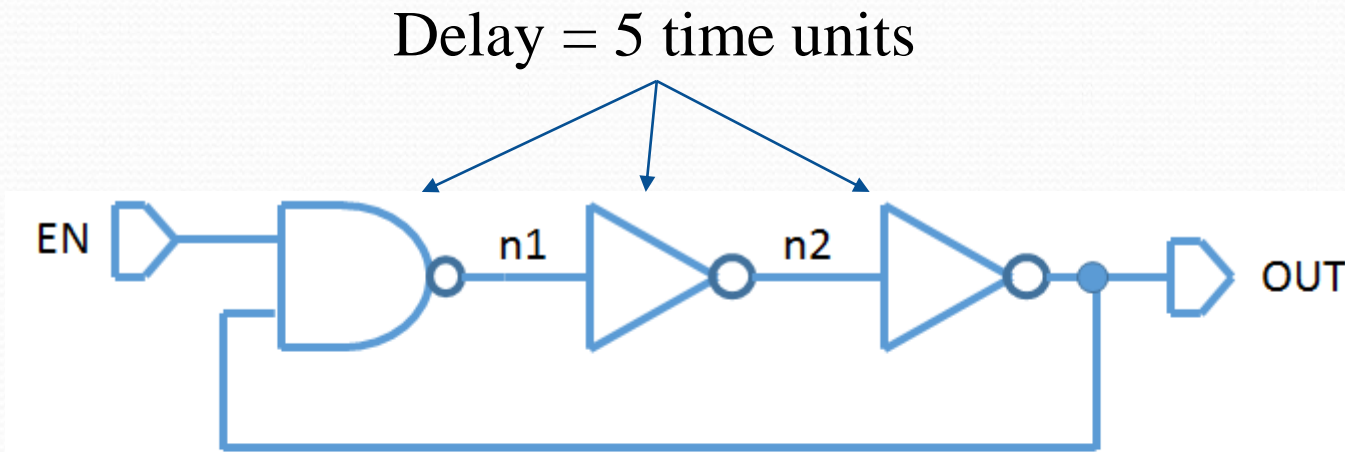Exercise 2: Structural Verilog *(implement ring oscillator)*



- What does this circuit do when you raise EN?
- Assume EN has been low for a while. Then simulate (in your head) what happens when EN is raised.
- Create a test bench *(see next slide)* to instantiate and test it.
 - EN should be low for 15 time units then raised

Exercise 2: Testbench Basics

- At a minimum a testbench has to do 3 things:
 1. Instantiate the DUT
 2. Hook up the DUT
 3. Apply stimulus to DUT inputs

```
module basic_test_bench();                                // a testbench is self-contained (has no inputs/outputs)

reg stim1, stim2;                                         // stimulus to DUT declared as type reg or logic

// Instantiate DUT = Device Under Test //
DUT_module iNAME(.clk(clk), .rst_n(rst_n), .in1(stim1), .in2(stim2), .out1());

initial begin                                             // stimulus typically provided in an initial block
    stim1 = 0;
    stim2 = 1;
    #5;                                                    // wait 5 time units then change stimulus
    stim1 = 1;
    #5 $stop();                                           // wait 5 more time units then stop the simulation
end

endmodule
```

module name of DUT
Does not have to match file name

Instance name can be anything, but is required

Input of DUT named in1 is hooked to a signal called stim1 at this level of hierarchy

Outputs of DUT can be hooked to nothing, however, more likely you would hook it to a signal so you can monitor it

Exercise 2: Testbench Basics

- Create the DUT using structural verilog (**ring_osc.sv**)
- Create a test bench (**ring_osc_tb.sv**) to instantiate and test it.
 - **EN** should be low for 15 time units then raised
- Capture the waveforms (**waves.jpg**) proving it works
- Submit **ring_osc.sv**, **ring_osc_tb.sv**, and **waves.jpg** to the dropbox for Ex02