

ECE 551

Digital Design And Synthesis

Fall '21

case statements
Proper SM Coding
Random Misc Stuff

1

Administrative Matters

- Cummings paramdesign paper for hdlcon (posted on class website)
- HW3 Posted (*a difficult one*)
- Midterm I
 - Weds Oct 7th @ classtime.

2

case Statements

- System Verilog has four types of case statements:
 - case, casex, casez, & case () inside**
- Performs bitwise match of expression and case item
 - Both must have same bitwidth to match!
- case**
 - Can detect **x** and **z**! (good for testbenches & when no wildcards needed)
- casez & casex**
 - Used **x**, **z**, **?** As wild cards, but in both case item & case expression. made them error prone, obsoleted by **case () inside**.
- case () inside**
 - Uses **x**, **z**, and **?** as “don’t care” bits (in case items only). This is good for decoding instructions where some bits are don’t care.

3

case statement (general form)

```

case (expression)
  alternative1 : statement1;           // any of these statements could
  alternative2 : statement2;           // be a compound statement using
  alternative3 : statement3;           // begin/end
  default : statement4                 // always use default for synth stuff
endcase

```

```

localparam AND = 2'b00;
localparam OR = 2'b01;
localparam XOR = 2'b10;

always_comb
  case (alu_op)
    AND      : alu = src1 & src2;
    OR       : alu = src1 | src2;
    XOR      : alu = src1 ^ src2;
    default  : alu = src1 + src2;
  endcase

```

Why always have a default?

Same reason as always having an else with an if statement.

All cases are specified, therefore no unintended latches.

4

case statement (improved example)

```
typedef enum logic [1:0] {AND, OR, XOR, ADD} alu_op_t;

alu_op_t alu_op_i;
alu_op_i = alu_op_t'(alu_op);

always_comb
case (alu_op_i)
  AND      : alu = src1 & src2;
  OR       : alu = src1 | src2;
  XOR      : alu = src1 ^ src2;
  default  : alu = src1 + src2;
endcase
```

If **alu_op** was a port/signal of type **alu_op_t** already, then this casting to intermediate **alu_op_i** would not be necessary.

Use of enum type makes debug easier because waveforms display as names (AND,OR,XOR), not encoded values.

alu_op_i 

5

Using case To Detect x And z

- Only use this functionality in a testbench!

```
case (sig)
  1'bz:    $display("Signal is floating.");
  1'bx:    $display("Signal is unknown.");
  default: $display("Signal is %b.", sig);
endcase
```

6

casex Statement

- Uses x, z, and ? as single-bit wildcards in case item and expression
- Uses first match encountered

```
always @(op_code) begin
  casex (op_code) // case expression
    2'b0?: control = 8'b00100110; // case item1
    2'b10: control = 8'b11000010; // case item 2
    2'b11: control = 8'b00111101; // case item 3
    default: $display("opcode invalid");
  endcase
end
```

- What is the output for code = 2'b01
- What is the output for code = 2'b1x

7

```
always_comb begin
  casex (case_exp)
    3'b0?: $display("case1");
    3'b10?: $display("case2");
    3'b111: $display("case3");
    default: $display("default case");
  endcase
end
```

```
always_comb begin
  case (case_exp) inside
    3'b0?: $display("case1");
    3'b10?: $display("case2");
    3'b111: $display("case3");
    default: $display("default case");
  endcase
end
```

8

8

case () inside Statement

- Uses x, z, and ? as single-bit wildcards in **case item only**

```
always_comb begin
  case (thumb_opcode) inside
    6'h001???: begin // thumb LD/ST direct+imm
      ...
    6'b00????: begin // thumb immediate instructions
      ...
    6'b0101??: begin // thumb LD/ST indirect
      ...
    endcase
  end
```

Might be good to remember this if you take 552 or 554

- case () inside** really shines when performing instruction decoding for most processor ISA's.
- This example shows a possible decode of a few ARM thumb opcodes.

9

9

Use of Range with case () inside

```
always_comb
  case (graduation_range) inside
    [1950:1959] : $display("Did you kiss at the drive in?");
    [1960:1969] : $display("What was tripping on LST like?");
    [1970:1979] : $display("Are you sad disco died?");
    [1980:1989] : $display("How big was your hair back then?");
    [1990:1999] : $display("Were you hip hop or grunge?");
  endcase
```

- This range checking is synthesizable and could also be useful in decode applications.

10


10

How Does a case(x) Statement Synthesize?


Remember the First Match is taken
(there is an inferred priority)

```
always_comb
  case (sel)
    2'b00 : out = a;
    2'b01 : out = b;
    default : out = c;
  endcase
```

Synthesis Tool

 

or this?

 

Depends on several factors including some synthesis directives. However the 2nd case is what we expect it to do without any directives. System verilog gives us more control.

11


11

System Verilog Case Options

unique means one and only one case will match. So can synthesize it flat

```
always_comb
  unique case (sel)
    2'b00 : out = a;
    2'b01 : out = b;
    default : out = c;
  endcase
```

Synthesis Tool

 

```
always_comb begin
  nxt_state = state1hot;
  unique case (1'b1)
    state1hot[0] : nxt_state = 3'b010;
    state1hot[1] : nxt_state = 3'b100;
    state1hot[2] : nxt_state = 3'b001;
  endcase
end
```

This would throw a warning in synthesis because it clearly does not cover all cases


This would also throw a warning in simulation if **state1hot** was 3'b111 because multiple conditions would match

12

System Verilog Case Options

priority tells the synthesizer *and simulator* that at least one of the cases will always match
 
```
always_comb begin
  out = c;
  priority case (sel)
    2'b00 : out = a;
    2'b01 : out = b;
    2'b10 : out = c;
  endcase
end
```




This would throw a warning in simulation if **sel** was 2'b11 because it does not match any case item.

13

13

State Machines

 

State Machines:

- Next State and output logic are combinational blocks, which have outputs dependent on the current state.
- The current state is, of course, stored by a FF.


What is the best way to code State Machines?:

- Best to separate combinational (blocking) from sequential (non-blocking)
- Output logic and state transition logic can be coded in same **always** block since they have the same inputs
- Output logic and state transition logic are ideally suited for a **case** statement

14

14

State Diagrams

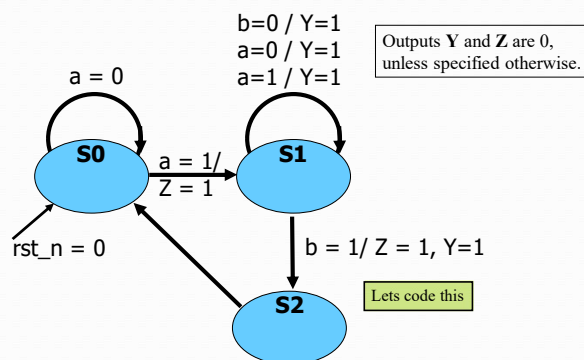

15

15

SM Coding

```
module fsm(clk,rst_n,a,b,Y,Z);
  input clk,rst_n,a,b;
  output reg Y,Z;
  typedef enum reg [1:0] {S0, S1, S2} state_t;

  state_t state,next_state;

  always_ff @(posedge clk,
    negedge rst_n)
    if (!rst_n)
      state <= S0;
    else
      state <= next_state;
```


What problems do we have here?

```
always_comb
  case (state)
    S0 : if (a) begin
      next_state = S1;
      Z = 1; end
    else
      next_state = S0;
    S1 : begin
      Y=1;
      if (b) begin
        next_state = S2;
        Z=1; end
      else
        next_state = S1;
      end
    S2 : next_state = S0;
  endcase
endmodule
```

16

16

SM Coding (2nd try of combinational)

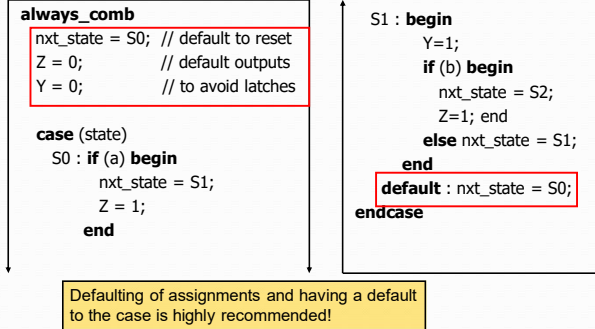

17

17

SM Coding Guidelines


- 1) Keep state assignment in separate **always_ff** block using non-blocking "<=" assignment
- 2) Code state transition logic and output logic together in a **always_comb** block using blocking assignments
- 3) Assign default values to all outputs, and the **nxt_state** registers. This helps avoid unintended latches
- 4) Remember to have a default to the case statement.
 - Default should be (if possible) a state that transitions to the same state as reset would take the SM to.
 - Avoids latches
 - Makes design more robust to spurious electrical/cosmic events.

18

18

SM Interacting with SM

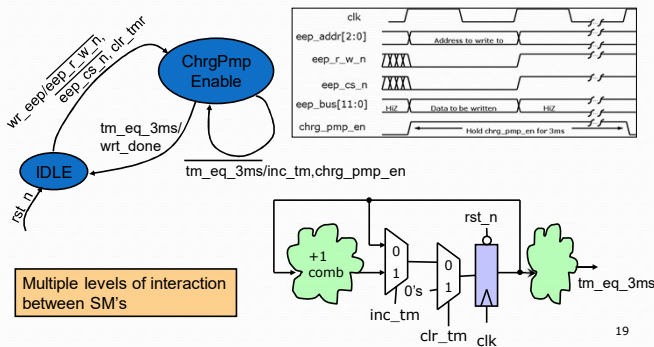- A very common case is a state that needs to be held for a certain time.
 - ✓ The state machine in this case may interact with a timer (counter).



19

19

EEPROM Write SM Example [1]

```

module eeprom_sm(clk,rst_n,wrt_eep,
wrt_data,eep_r_w_n,eep_cs_n,
eep_bus,chrp_pmp_en,wrt_done);

//// implement 3ms timer below ////
always_ff @(posedge clk, negedge rst_n)
if (!rst_n) tm <= 21'h000000;
else if (clr_tm) tm <= 21'h000000;
else if (inc_tm) tm <= tm+1;

input clk,rst_n,wrt_eep;
input [11:0] wrt_data; // data to write
output eep_r_w_n,eep_cs_n;
output chrg_pmp_en; // hold for 3ms
inout [11:0] eep_bus;

//// @500MHZ cnt of 16E360 => 3ms ////
assign tm_eq_3ms = (tm==21'h16E360) ?
1'b1 : 1'b0;

typedef enum reg {IDLE,
CHRG} state_t;
state_t state, nxtState;
reg [20:0] tm; // 3ms ==> 21-bit timer
reg clr_tm, inc_tm, bus_wrt;

//// implement state register below ////
always_ff @(posedge clk or
negedge rst_n)
if (!rst_n) state <= IDLE;
else state <= nxtState;
    
```

20

20

EEPROM Write SM Example [2]

```

//// state transition logic & ////
//// output logic ////
always_comb begin
    nxtState = IDLE; // default all
    bus_wrt = 0; // to avoid
    clr_tm = 0; // unintended
    inc_tm = 0; // latches
    chrg_pmp_en = 0;

    case (state)
        IDLE : if (wrt_eep) begin
            clr_tm = 1;
            bus_wrt = 1;
            nxtState = CHRNG;
        end
    endcase

    default : begin // is CHRNG
        inc_tm = 1;
        chrg_pmp_en = 1;
        if (tm_eq_3ms)
            begin
                wrt_done = 1;
                nxtState = IDLE;
            end
        else
            nxtState = CHRNG;
    end
end

assign eep_r_w_n = ~bus_wrt;
assign eep_cs_n = ~bus_wrt;
assign eep_bus = (bus_wrt) ?
    wrt_data : 12'bzzz;
endmodule

```

21

The Beauty of the Enumerated type

- One construct old school verilog was missing was an enumerated type.
- For state definition we use **localparam** was used for code readability

```

localparam IDLE = 2'b00;
localparam CONV = 2'b01;
localparam ACCM = 2'b10;

```

However, in waveform viewing it still shows up as digits. One has to always refer back to the encoding while debugging.

state 00 01 10 01

- System verilog corrected this by adding an enumerated type.

```

typedef enum reg [1:0] { IDLE, CONV, ACCM } state_t;
state_t state, nxt_state; // declare state and nxt_state signals

```

state IDLE CONV ACCM CONV


Makes debug much easier

22

22

UART Wrapper

 
- Consider This Application. Collecting 3-bytes from a UART receiver and packaging them into a 24-bit command.



23

23

UART Wrapper Bubble Diagram

 

24

24

SM in System Verilog

```

module UART_wrapper_sm(input clk, rst_n, ...
typedef enum reg [1:0] {HIGH,MID,LOW} state_t;
state_t state, nxt_state;

logic capture_high,capture_mid,set_cmd_rdy,
clr_cmd_rdy,clr_rdy;

////////// infer state flops //////////
always_ff @(posedge clk, negedge rst_n)
if (rst_n)
    state <= HIGH;
else
    state <= nxt_state;

always_comb begin
    ////////// default outputs //////////
    capture_high = 0;
    capture_mid = 0;
    set_cmd_rdy = 0;
    clr_cmd_rdy = 0;
    clr_rdy = 0;
    nxt_state = HIGH;
end

```

```

case (state)
    MID : if (rdy) begin
        capture_mid = 1;
        clr_rdy = 1;
        nxt_state = LOW;
    end else
        nxt_state = MID;
    LOW : if (rx_rdy) begin
        set_cmd_rdy = 1;
        clr_rdy = 1;
        nxt_state = HIGH;
    end else
        nxt_state = LOW;
    ////////// default case = HIGH //////////
    default : if (rdy) begin
        capture_high = 1;
        clr_rdy = 1;
        clr_cmd_rdy = 1;
        nxt_state = MID;
    end
endcase
end

```

25

25

Default nxt_state to state

Allows less coding if a state is to remain in same state

```

module UART_wrapper_sm(input clk, rst_n, ...
typedef enum reg [1:0] {HIGH,MID,LOW} state_t;
state_t state, nxt_state;

logic capture_high,capture_mid,set_cmd_rdy,
clr_cmd_rdy,clr_rdy;

////////// infer state flops //////////
always_ff @(posedge clk, negedge rst_n)
if (rst_n)
    state <= HIGH;
else
    state <= nxt_state;

always_comb begin
    ////////// default outputs //////////
    capture_high = 0;
    capture_mid = 0;
    set_cmd_rdy = 0;
    clr_cmd_rdy = 0;
    clr_rdy = 0;
    nxt_state = state;
end

```

```

case (state)
    MID : if (rdy) begin
        capture_mid = 1;
        clr_rdy = 1;
        nxt_state = LOW;
    end else
        nxt_state = MID;
    LOW : if (rx_rdy) begin
        set_cmd_rdy = 1;
        clr_rdy = 1;
        nxt_state = HIGH;
    end else
        nxt_state = LOW;
    ////////// default case = HIGH //////////
    default : if (rdy) begin
        capture_high = 1;
        clr_rdy = 1;
        clr_cmd_rdy = 1;
        nxt_state = MID;
    end
endcase
end

```

26

26

End of Lecture05 Part I

27

27

Random Misc Topics


Next slides are a bunch of stuff I wasn't sure where to put, but seemed like good information.

28

28

Consider how a **case/if else** will synthesize

Synthesizing a non-parallel case

 

29

29

SystemVerilog – Control Constructs

- **unique** keyword modifier

unique case (sel)

CASE1: ...

CASE2: ...

CASE3: ...

endcase

- **unique** tells the synthesizer *and simulator* that **one, and only one, case** will be selected
- Also works with if: **unique if**(...) ...

30

30


unique if Example

```
always_comb begin
    capX = 1'b0;
    capY = 1'b0;
    unique if (X_accel < min_accel)
        capX = 1'b1;
    else if (Y_accel < min_accel)
        capY = 1'b1;
end
```

This example is not a good use of **unique if**. It is likely the both the X-axis and Y-axis accelerometer values could be less than the min_accel. In which case there would be a run-time warning thrown in simulation because the match is not unique.

```
always_comb begin
    unique if (read_SRAM)
        dst_bus = RAM_data;
    else if (read_EEP)
        dst_bus = EEP_data;
    else
        dst_bus = 16'hzzzz;
end
```

 This code would be a good use of **unique if** when you know read_EEP and read_SRAM are mutex



31

31

SystemVerilog – Control Constructs

- **priority** keyword modifier

priority case (sel)

CASE1: ...

CASE2: ...

endcase

- **priority** tells the synthesizer *and simulator* that **at least one of the cases will always match**. If this doesn't happen in simulation it will warn you.
- Also works with if: **priority if**(...) ...

32

32

priority if Example

```

always_comb
priority if (X_accel < min_accel) begin
    capX = 1'b1;
    capY = 1'b0;
end else if (Y_accel < min_accel) begin
    capX = 1'b0;
    capY = 1'b1;
end

```

This will synthesize as shown, and would throw a run-time warning if neither X_accel or Y_accel were less than min_accel

```

always_comb begin
    priority if (read_SRAM)
        dst_bus = RAM_data;
    else if (read_EEPROM)
        dst_bus = EEPROM_data;
    else
        dst_bus = 16'hzzzz;
end

```

This would synthesize as shown. **priority if**'s will throw a run-time warning if no conditions match, but since this code has a pure **else** that will not happen.

33

Encoder With case

```

module encoder (output reg [2:0] Code, input [7:0] Data);
always @ (Data)
    // encode the data
    case (Data)
        8'b00000001 : Code = 3'd0;
        8'b00000010 : Code = 3'd1;
        8'b00000100 : Code = 3'd2;
        8'b00001000 : Code = 3'd3;
        8'b00010000 : Code = 3'd4;
        8'b00100000 : Code = 3'd5;
        8'b01000000 : Code = 3'd6;
        8'b10000000 : Code = 3'd7;
        default : Code = 3'bxxx; // invalid, so don't care
    endcase
endmodule

```

How do we think it will synthesize?

34

Priority Encoder With case () inside

```

module priority_encoder (output reg [2:0] Code, input [7:0] Data);
always_comb // encode the data
    case (Data) inside
        8'b1xxxxxxx : Code = 7;
        8'b01xxxxxx : Code = 6;
        8'b001xxxxx : Code = 5;
        8'b0001xxxx : Code = 4;
        8'b00001xxx : Code = 3;
        8'b000001xx : Code = 2;
        8'b0000001x : Code = 1;
        8'b00000001 : Code = 0;
        default : Code = 3'bxxx;
    endcase
endmodule

```

Will this synthesize larger or smaller than the previous example?

35

Seven Segment Display

```

module Seven_Seg_Display (Display, BCD, Blanking);
    output reg [6: 0] Display; // abc_defg
    input [3: 0] BCD;
    input Blanking;

    localparam BLANK = 7'b111_1111; // active low
    localparam ZERO = 7'b000_0001; // h01
    localparam ONE = 7'b100_1111; // h4f
    localparam TWO = 7'b001_0010; // h12
    localparam THREE = 7'b000_0110; // h06
    localparam FOUR = 7'b100_1100; // h4c
    localparam FIVE = 7'b010_0100; // h24
    localparam SIX = 7'b010_0000; // h20
    localparam SEVEN = 7'b000_1111; // h0f
    localparam EIGHT = 7'b000_0000; // h00
    localparam NINE = 7'b000_0100; // h04

```

Defined constants – can make code more understandable!

36

Seven Segment Display [2]

```
always @ (BCD or Blanking)
if (Blanking) Display = BLANK;
else
case (BCD)
4'd0:      Display = ZERO;
4'd1:      Display = ONE;
4'd2:      Display = TWO;
4'd3:      Display = THREE;
4'd4:      Display = FOUR;
4'd5:      Display = FIVE;
4'd6:      Display = SIX;
4'd7:      Display = SEVEN;
4'd8:      Display = EIGHT;
4'd9:      Display = NINE;
default:   Display = BLANK;
endcase
endmodule
```

*Using the
defined
constants!*

37

37

Mixing Flip-Flop Styles (1)

- What will this synthesize to?


```
module badFFstyle (output reg q2, input d, clk, rst_n);
reg q1;

always @(posedge clk)
if (!rst_n)
q1 <= 1'b0;
else begin
q1 <= d;
q2 <= q1;
end
endmodule
```

38

38

Mixing Flip-Flop Styles (2)

 

It synthesizes like this right?

```
module badFFstyle (output reg q2,
input d, clk, rst_n);
reg q1;


always @(posedge clk)
if (!rst_n)
q1 <= 1'b0;
else begin
q1 <= d;
q2 <= q1;
end
endmodule
```

If !rst_n then q2 is not assigned...
It has to keep its prior value

39

39

Mixing Flip-Flop Styles (3)

 

```
module badFFstyle (output reg q2,
input d, clk, rst_n);
reg q1;

always @(posedge clk)
if (!rst_n)
q1 <= 1'b0;
q2 <= q2;
else begin
q1 <= d;
q2 <= q1;
end
endmodule
```

40

40

Mixing Flip-Flop Styles (4)

```

module goodFFstyle (output reg q2, input d, clk, rst_n);
  reg q1;

  always @(posedge clk)
    if (!rst_n) q1 <= 1'b0;
    else q1 <= d;

  always @(posedge clk)
    q2 <= q1;
endmodule

```

Only combine like flops (same reset structure) in a single **always** block.

If their reset structure differs, split into separate **always** blocks as shown here.

41

41

Eric's Coding Guideline

- Unless flops have the same conditions under which they are reset and enabled separate them into different **always** blocks.

42

42

Inter vs Intra Statement Delays

- Inter-assignment delays block both evaluation and assignment
 - #4 c = d;
 - #8 e = f;
- Intra-assignment delays block assignment but not evaluation
 - c = #4 d;
 - e = #8 f;
- Blocking statement is still blocking though, so evaluation of next statements RHS still does not occur until after the assignment of the previous expression LHS.
 - What?? How is it any different then? Your confusing me!

43

43

Inter vs Intra Statement Delays (Blocking Statements)

```

module inter();
  integer a,b;
  initial begin
    a=3;

    #6 b = a + a;
    #4 a = b + a;
  end
endmodule

```

Compare these two modules

```

module intra();
  integer a,b;
  initial begin
    a=3;

    b = #6 a + a;
    a = #4 b + a;
  end
endmodule

```

Time	Event
0	a=3
6	b=6
10	a=9

Yeah, Like I said, they are the same!
Or are they?

Time	Event
0	a=3
6	b=6
10	a=9

44

44

Intra Statement Delays (Blocking Statements)

```

module inter2();
integer a,b;
initial begin
a=3;
#6 b = a + a;
#4 a = b + a;
end
initial begin
#3 a=1;
#5 b=3;
end
endmodule

```

Time	Event
0	a=3
3	a=1
6	b=2
8	b=3
10	a=4

```

module inter2();
integer a,b;
initial begin
a=3;
b = #6 a + a;
a = #4 b + a;
end
initial begin
#3 a=1;
#5 b=3;
end
endmodule

```

Time	Eval Event	Assign Event
0	next_b=6	a=3
3	--	a=1
6	next_a=7	b=6
8	--	b=3
10	--	a=7

45

Non-Blocking: Inter-Assignment Delay

- Delays both the evaluation and the update...effectively becomes a blocking statement

```

always @(posedge clk) begin
b <= a + a;
#5 c <= b + a;
#2 d <= c + a;
end
initial begin
a = 3; b = 2; c = 1;
end

```

Time	Event
0	clk pos edge
0	b=6
5	c=9
7	d=12

46

Non-Blocking: Intra-Assignment Delay

- Delays the update, but not the evaluation.
Does not block

```

always @(posedge clk) begin
b <= a + a;
c <= #5 b + a;
d <= #2 c + a;
end
initial begin
a = 3; b = 2; c = 1;
end

```

Time	Event
0	clk pos edge
0	b=6
2	d=4
5	c=5

This is more like modeling the Clk2Q delay of a Flop
(it captures on rising edge, but has a delay till output)

47

Intra-Assignment Review

```

module bnb;
reg a, b, c, d, e, f;
initial begin // blocking assignments
a = #10 1; // a will be assigned 1 at time 10
b = #2 0; // b will be assigned 0 at time 12
c = #4 1; // c will be assigned 1 at time 16
end
initial begin // non-blocking assignments
d <= #10 1; // d will be assigned 1 at time 10
e <= #2 0; // e will be assigned 0 at time 2
f <= #4 1; // f will be assigned 1 at time 4
end
endmodule

```

Note: In testbenches I mainly find blocking inter-assignment delays to be the most useful. Delays really not used outside of testbenches that much during the design process.

48